

Chapter 2

Selected Elements of Digital Logic [Reading Only]

Chapter Objectives

- This chapter covers:
 - Quick review of digit logic components (adder, decoder, MUX, FF, registers, counters, etc.)
 - Most parts of this section are self-study from EE232 or other online Digital logic resources
 - Only the key materials will be reviewed
 - Memory Architecture
 - RAM, Address multiplexing, SRAM, DRAM
 - ROM types, programming

Self Study

- Number system and conversion
 - Binary, Decimal, Hexadecimal, Octal, BCD, code conversion (BCD to Gray, Hex to BCD, etc.)

- Hexadecimal Number System
 - Base 16
 - 16 possible symbols
 - 0-9 and A-F (A=10, B=11,..., F=15)
 - Allows for convenient handling of long binary strings

Decimal	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Hexadecimal	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
Binary	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111

Hexadecimal Number System

- Convert from **hex to decimal** by multiplying each hex digit by its positional weight

Example: $163_{16} = (?)_{10}$

$$\begin{aligned} 163_{16} &= 1 \times (16^2) + 6 \times (16^1) + 3 \times (16^0) \\ &= 1 \times 256 + 6 \times 16 + 3 \times 1 \\ &= 355_{10} \end{aligned}$$

- Convert from **decimal to hex** by using the repeated division method used for decimal to binary conversion
 - Divide the decimal number by 16
 - The first remainder is the LSB and the last is the MSB
- **How about HEX – BIN?**

Hexadecimal Number System

- In Hex, each digit ranges from 0-15, i.e. 4 binary bits are required to represent it

Decimal	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Hexadecimal	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
Binary	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111

- Example of hex to binary conversion:

- $(9F2)_{16} = (?)_2 \longrightarrow (1001_1111_0010)_2$

- Convert from binary to hex :

- By grouping bits in four starting with the LSB
 - Each group is then converted to the hex equivalent
 - Zeros are added to the left of the MSB to fill out the last group

- Example: $(1110100110)_2 = (?)_{16} \longrightarrow (11_1010_0110)_2 = (3A6)_{16}$

Examples: Binary Representation

□ 6-bit representation

	<div>+16</div> <div>Sign Magnitude</div>	<div>-16</div> <div>Sign Magnitude</div>
Un-signed Magnitude	$\overbrace{0}^{\text{Sign}} \overbrace{10000}^{\text{Magnitude}}$	$\overbrace{0}^{\text{Sign}} \overbrace{10000}^{\text{Magnitude}}$
Signed Magnitude	010000	110000
1's Complement	010000	101111
2's Complement	010000	110000

Q. How to extend the representation for 8-bit?



Examples: Binary Representation

□ 8-bit representation

	+115	-115
Un-signed Magnitude	01110011	01110011
Signed Magnitude	01110011	11110011
1's Complement	01110011	10001100
2's Complement	01110011	10001101

Arithmetic/Logic Unit (ALU)

 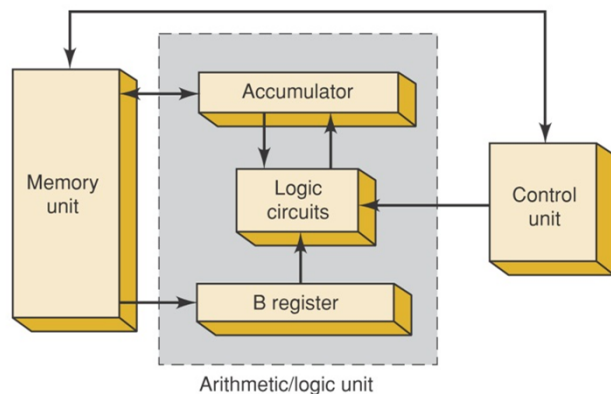- All arithmetic operations take place in the ALU of a computer



A = 4-bit input number
 B = 4-bit input number
 C_N = carry into LSB position
 S = 3-bit operation select inputs
 F = 4-bit output number
 C_{N+4} = carry out of MSB position
 OVR = overflow indicator

Function Table

S_2	S_1	S_0	Operation	Comments
0	0	0	CLEAR	$F_3F_2F_1F_0 = 0000$
0	0	1	B minus A	Needs $C_N = 1$
0	1	0	A minus B	
0	1	1	A plus B	Needs $C_N = 0$
1	0	0	$A \oplus B$	Exclusive-OR
1	0	1	$A + B$	OR
1	1	0	AB	AND
1	1	1	PRESET	$F_3F_2F_1F_0 = 1111$

Notes: S inputs select operation.
 OVR = 1 for signed-number overflow.




(b)

Example: Determine the output for the following sequence: (a) $S_2S_1S_0 = 010$, $A_3A_2A_1A_0 = 0100$, $B_3B_2B_1B_0 = 0001$, $C_N = 1$

   (b) Change select code to 011, and redo

Propagation Delay / Critical Path

- The maximum time when an input changes until the outputs reach their final values - t_p
- Typical values are in the picoseconds (10^{-12}) range






Critical Path: The longest delay from input to final output ($10 + 15 + 20 = 45ps$)

The significance is that X reacts to the change in A after 45ps

Flip-Flop (or sometimes Latch)

   - The **flip-flop**, abbreviated as **FF**, is a key memory element (stores **1 bit** => 1 FF = 1 bit)
- Sequential Elements:
 - Everything changes in accordance with **clock signal level** or **transitions**
- Latch: Storage elements that operate (change output levels) with **signal levels**
- Flip-Flop: Storage elements that operate with **clock (or signal) transitions**




Source: Digital Systems: Principles and Applications, Tocci, Widmer and Moss, 10E, ISBN: 0131725793

Latch Structure

SET = 1 $\Rightarrow Q = 1$


RESET = 1 $\Rightarrow Q = 0$

 


a) Clocked S-R latch

Inputs			Output
S	R	CLK	Q
0	0	\uparrow	Q_0 (no change)
1	0	\uparrow	1
0	1	\uparrow	0
1	1	\uparrow	Ambiguous

 Q_0 is output level prior to \uparrow of CLK.
 \downarrow of CLK produces no change in Q.





Dr. KHAN WAHID
 2012-13 (Term 1)

 

b) Basic S-R Latch

Set	Reset	Output
1	1	No change
0	1	$Q = 1$
1	0	$Q = 0$
0	0	Invalid*


*Produces $Q = \bar{Q} = 1$.

  

c) Basic S-R Latch

Set	Reset	Output
0	0	No change
1	0	$Q = 1$
0	1	$Q = 0$
1	1	Invalid*

*Produces $Q = \bar{Q} = 0$.


 


Source: Digital Design, Mano and Ciletti, 4E, ISBN: 0131989243


Latch vs. Flip-Flop

□ Latch: Level sensitive


□ Flip-Flop: Edge sensitive

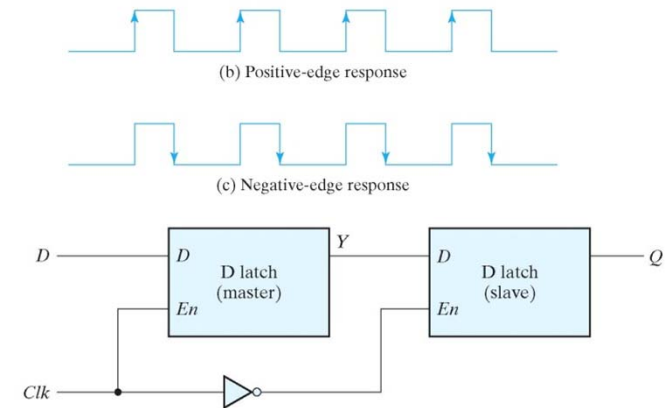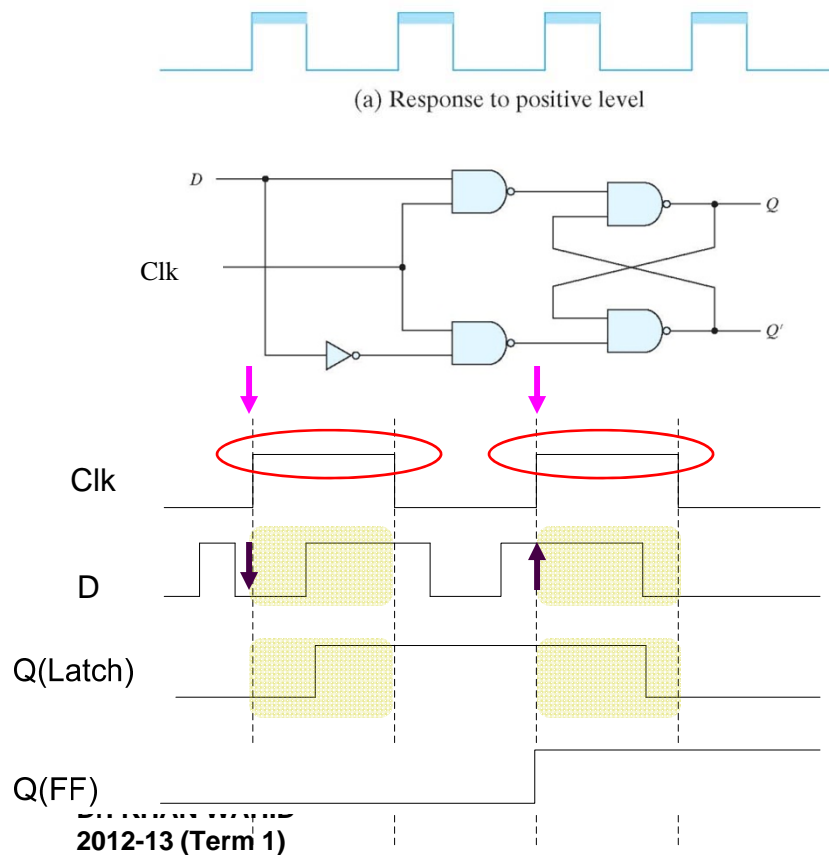

Or

 

Compare: Level vs. Edge




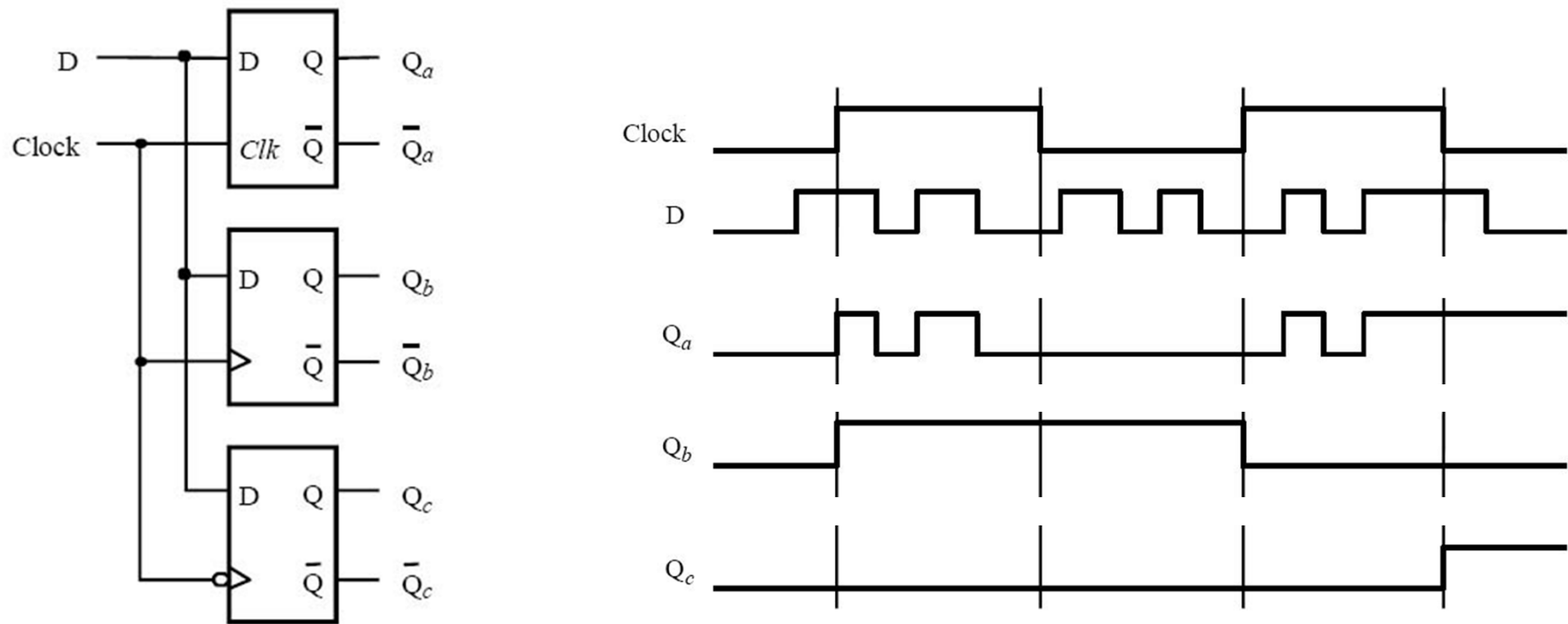


Source: *Fundamentals of Digital Logic with Verilog Design*, Brown and Vranesic, 2E, ISBN: 9780073380339

Problems with Latches (level sensitive)




□ Example: Two D-Latches are in series

 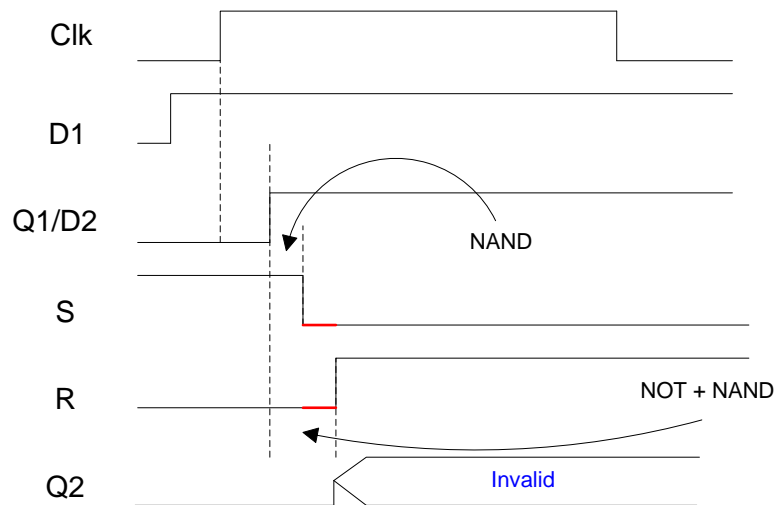  

Dr. KHAN
2012-13 (T) Clk pulse is too wide


Clk pulse is too narrow

 Increasingly better bit storage: SR Latch to Edge-triggered DFF




Feature: $S=1$ sets Q to 1, $R=1$ resets Q to 0.

Problem: $SR=11$ yield undefined Q .

 


Feature: S and R only have effect when $C=1$. We can design outside circuit so $SR=11$ never happens when $C=1$.

 Problem: avoiding $SR=11$ can be a burden.



Feature: SR can't be 11 if D is stable before and while $C=1$, and will be 11 for only a brief glitch even if D changes while $C=1$.

 Problem: $C=1$ too long propagates new values through too many latches; too short may not enable a store.





Feature: Only loads D value present at rising clock edge, so values can't propagate to other flip-flops during same clock cycle. **Tradeoff:** uses more gates internally than D latch, and requires more external gates than SR — but gate count is less of an issue today.

Source: Digital Systems: Principles and Applications, Tocci, Widmer and Moss, 10E, ISBN: 0131725793

FF Timing Considerations

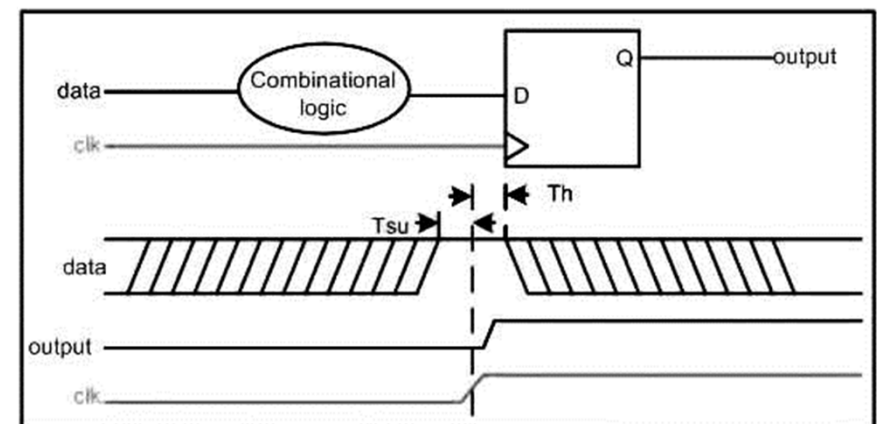 - FF are built from **gates and wires** – they will have **delays**.
Thus a real FF imposes some restrictions on when the FF's **input can change relative to CLK** so that correct operation is ensured
- **Setup Time:** D input must be stable before the clock edge (typ: 3ns) – **wait for D input**
- **Hold Time:** D input must be held stable after the clock edge (typ: 2ns) – **wait for CLK**



$$\text{Critical Window} = T_{su} + T_h$$

Metastability – How?

Set	Reset	Output
0	0	No change
1	0	$Q = 1$
0	1	$Q = 0$
1	1	Invalid*

*Produces $Q = \bar{Q} = 0$.

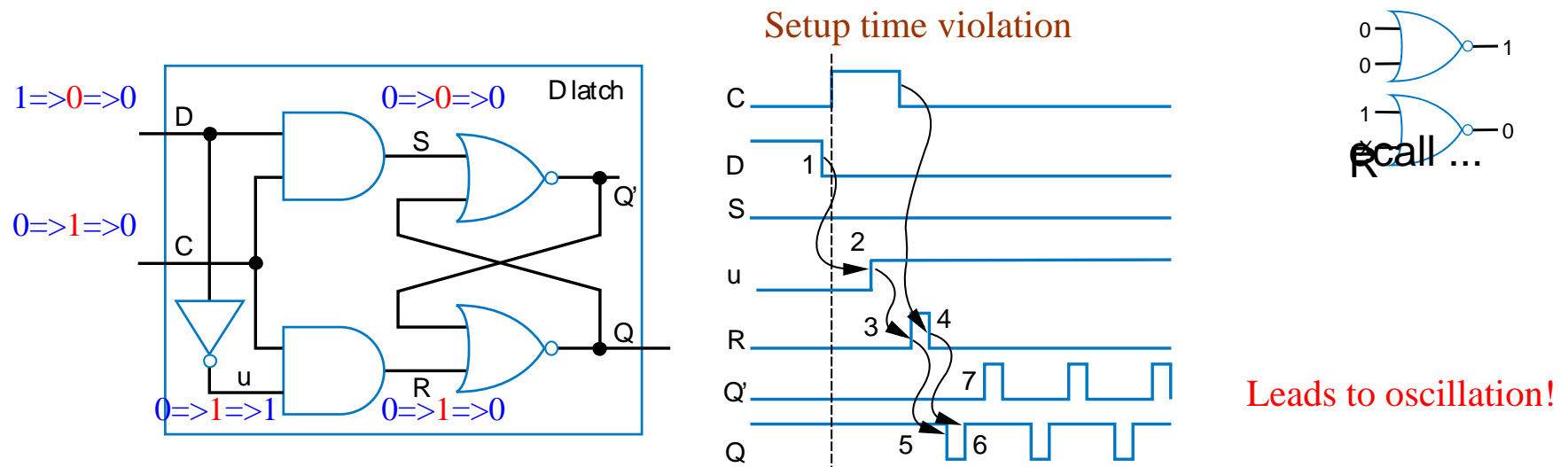




Figure 3.61 Setup time violation: D changed to 0 (1) too close to the rising clock. u changed to 1 after the inverter delay (2), and then R changed to 1 after the AND gate delay (3). But then the clock pulse was over, causing R to change back to 0 (4) before a stable feedback situation with $Q=0$ occurred in the cross-coupled NOR gates. R's change to 1 did cause Q to change to 0 after the NOR gate delay (5), but R's change back to 0 caused Q to change right back to 1 (6). The glitch of a 0 on Q fed back into the top NOR gate, causing Q' to glitch to 1 (7). That glitch of a 1 fed back to the bottom NOR gate, causing another glitch of a 0 on Q. That glitch runs around the cross-coupled NOR gate circuit (oscillation)—a race condition would eventually cause Q to settle to 1 or 0, or possibly enter a metastable state (to be discussed).

Metastability – When?

- If the circuit **violates setup and hold times** of a FF, the result is that the FF enters in a **metastable state** (other than stable 1 or stable 0 – sometimes referred as **quasi-stable state**)
- Cases when metastability occurs:
 - When a FF has an input that is not synchronized with the clock – **asynchronous input**
 - When the **clock's rise and fall time are too long** (i.e. more than the tolerable values)
 - When interfacing **two domains are operating at two different frequencies** or at the **same frequency but with different phase**
 - When the combinational **delay causes the flip-flop's data input to change inside the critical window**

Metastability – How to Prevent?

- Make sure that the clock period is long enough to allow for the resolution of quasi-stable states and for the delay of whatever logic may be in the path to the next flip-flop
- Add one or more successive synchronizing flip-flops as synchronizer which allows for an entire clock period (except for the setup time of the second flip-flop) for metastable events in the first synchronizing flip-flop to resolve themselves


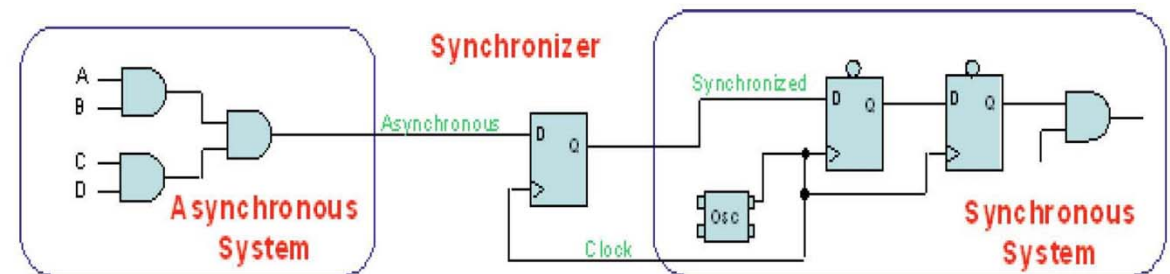
 


e.g., Other digital device

e.g., Microprocessor

Registers

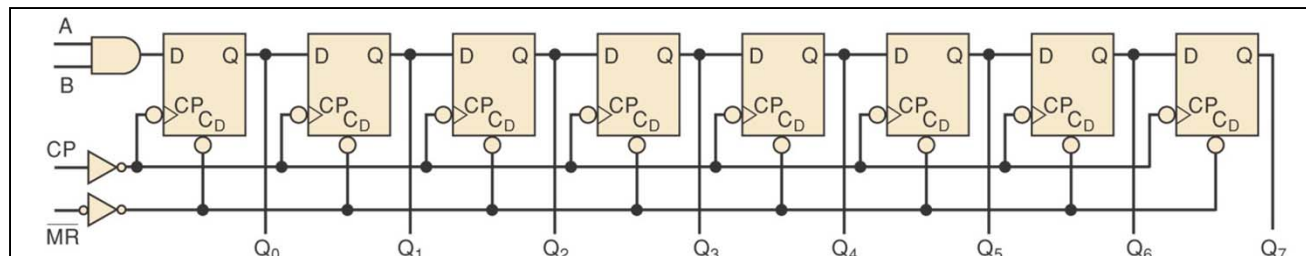  
- Registers are sets of flip-flops
 - Classified by the way data are entered and outputted
- Parallel in/parallel out (PIPO)
- Serial in/serial out (SISO)
- Parallel in/serial out (PISO)
- Serial in/parallel out (SIPO)




Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>

Register with Parallel Load

 

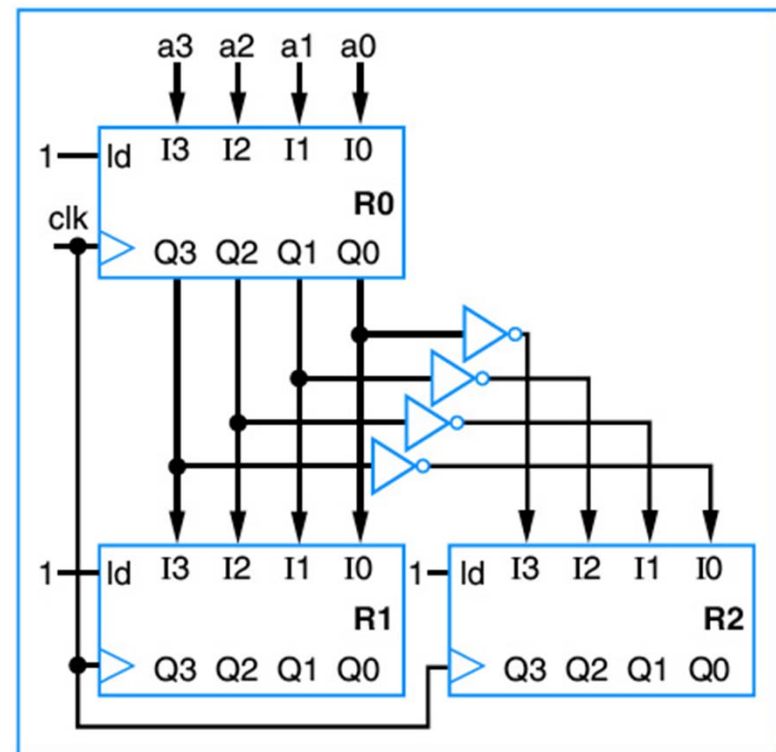load = 1 \Rightarrow parallel load @ CP
 load = 0 \Rightarrow hold current (no CP)




Example: Suppose the initial values of {a3,a2,a1,a0} are given. Find out the contents of R0, R1, and R3.

Source: Digital Design, Frank Vahid, 1st ed, 2006



<http://www.cs.ucr.edu/~vahid/dd>

Register with Parallel Load

 

Note that:

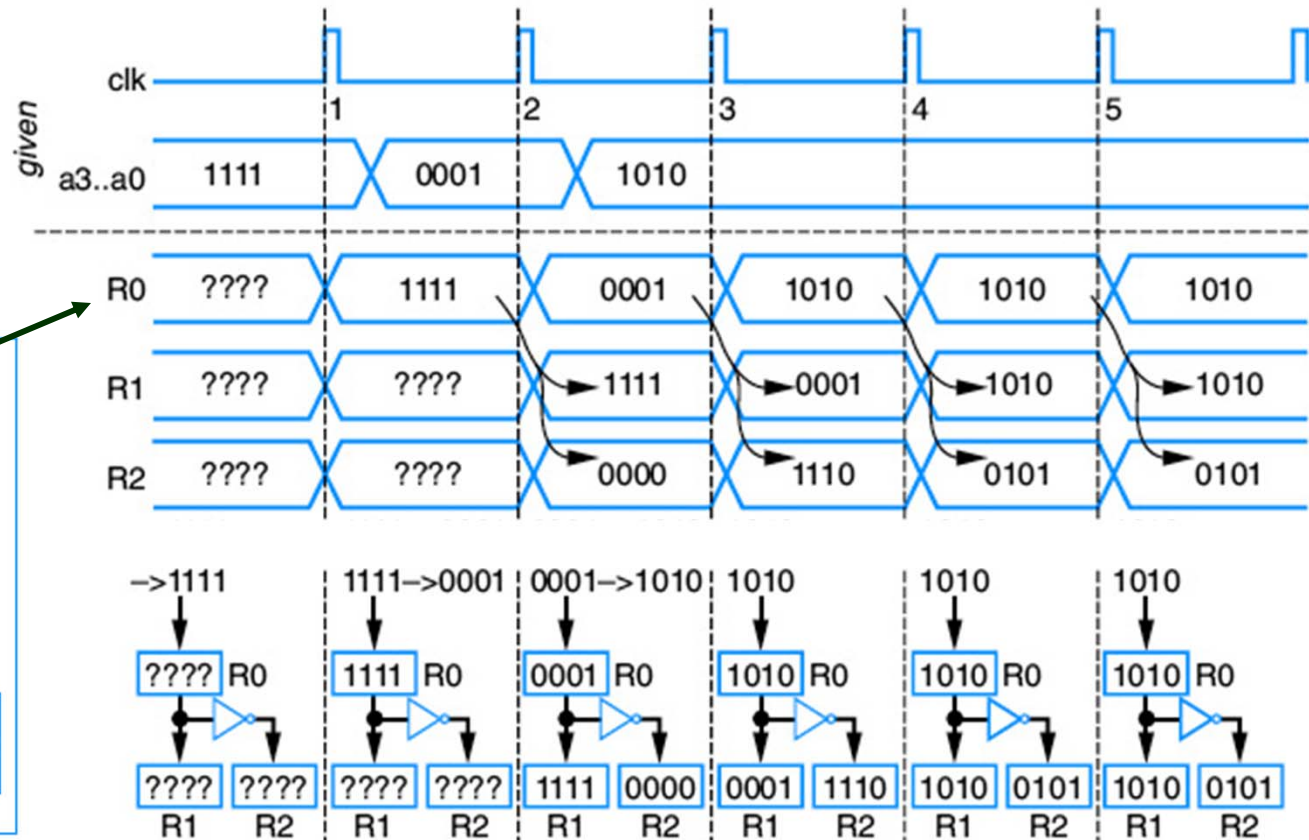 1. $ld = 1$ (for all)
2. $R2 = R1'$
3. Pay attention to $R0$ and $R1$





Important to note how the data are **latched** into registers at different clock edges – useful later in “**pipelining**”

Source: *Digital Systems: Principles and Applications*, Tocci, Widmer and Moss, 10E, ISBN: 0131725793

Memory Devices

 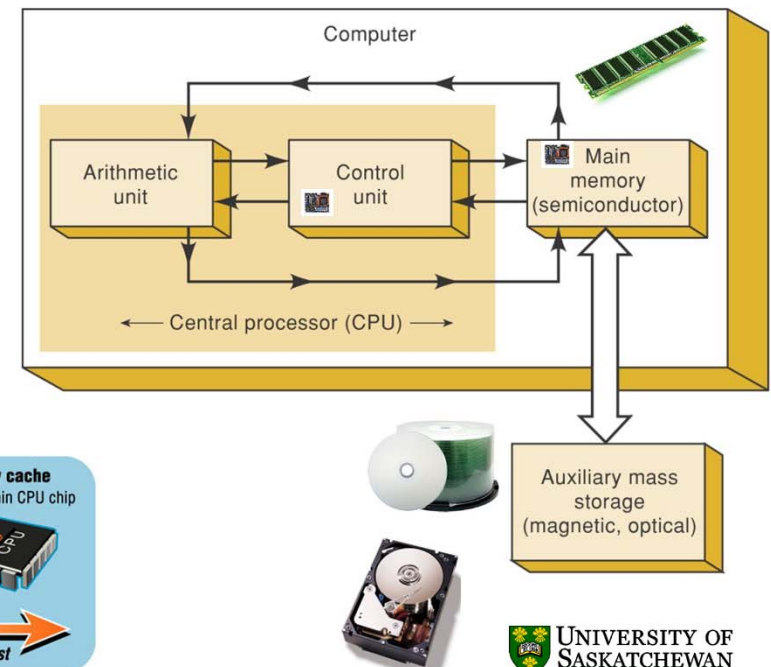- Memory: A device to which binary information is transferred for temporary storage and from which information is retrieved when needed for processing
- Commonly used memory devices:
 - Flip flops
 - Registers
 - RAM, ROM, etc.
- Cache memory:
 - Level 1 (L1), Level 2 (L2)
 - High-speed, small size



Memory Terminology

- **Memory cell:** An electrical circuit used to store a single bit
- **Memory word:** A group of bits
 - 1 byte = 8 bits; 1 nibble = 4 bits
- **Capacity:** Size of the memory cell
 - **16 x 4** => **16 words**, each word of **4 bits** => 64 bits = 8 bytes
 - 32 x 4 vs. 16 x 8
 - **Density** ⇔ Capacity
- **Address:** Each word in memory is assigned an identification number, called an address (for 64x4, how many address bits?)
- **Read:** Transfers binary information from a specific address out of memory
- **Write:** Transfers binary information into a specific address of memory



Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>

RAM vs. ROM

- Random Access Memory (RAM):
 - The architecture of the memory is such that **information can be retrieved from any locations** (or *addresses*) with the same time
 - Performs **both read and write**

  - Read Only Memory (ROM):
 - A memory device where **permanent binary information** is stored (used for storing program)
 - Once written, information **cannot be altered by write operation**
 - Performs **only read operation**




Source: *Digital Systems: Principles and Applications*, Tocci, Widmer and Moss, 10E, ISBN: 0131725793

Source: *Digital Design*, Mano and Ciletti, 4E, ISBN: 0131989243

A Typical Memory Cell

Each bit is one register

 

Control Inputs to Memory Chip

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

1024 words
(addresses or locations)

Memory address		Memory content
Binary	Decimal	
0000000000	0	10110101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101



1024 x 16 Memory

16 bits data
(contents)


Source: Digital Design, Mano and Ciletti, 4E, ISBN: 0131989243

A Typical Memory Cell

  - 1 cell = 1 bit = 1 register = 1 FF (S-R or D)



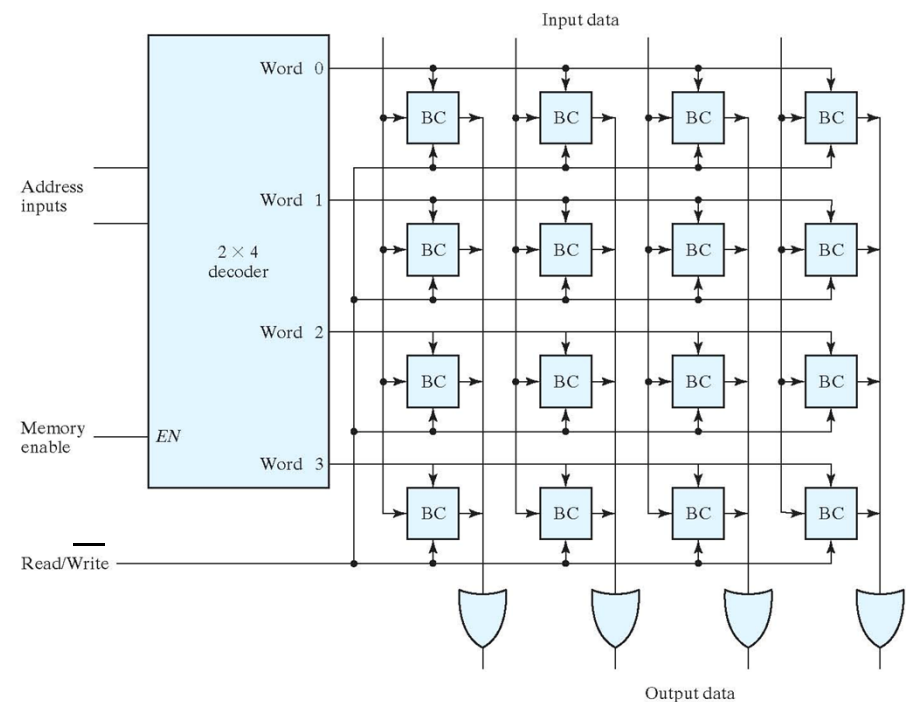Now very carefully note the operation for read and write – w.r.t. clock pulse??





4x4 RAM

Memory Timing Waveforms

- The operation of the memory unit is controlled by the CPU (synchronized by CPU's own internal clock)
 - No internal clock in memory – read and write operations are specified by control inputs (from the CPU)
 - The CPU provides these control signals in such a way to synchronize its internal clocked operations with the read and write memory operations
- Access time:
 - Time required to select a word and READ it
- Cycle time:
 - Time required to complete a WRITE operation

Source: Digital Design, Mano and Ciletti, 4E, ISBN: 0131989243


Memory Timing Waveforms

 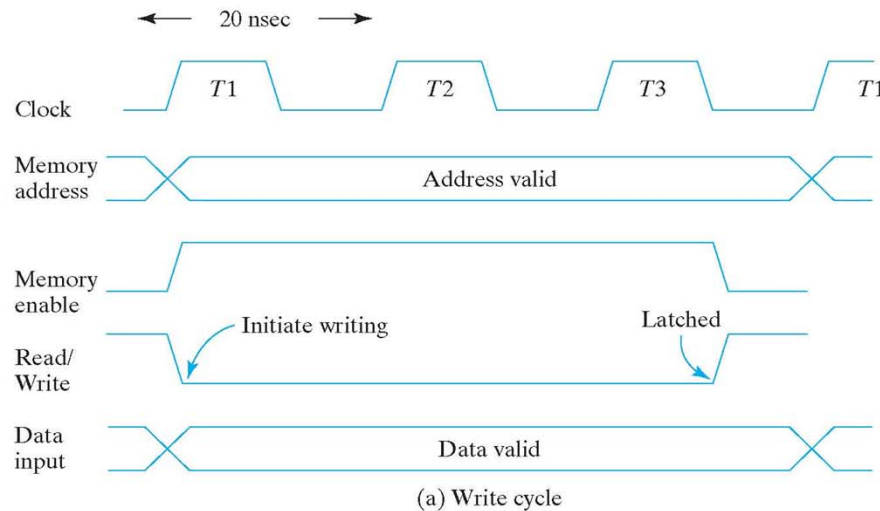

- Address and Data must be held constant until Data is latched

- Write operation needs CP to write data

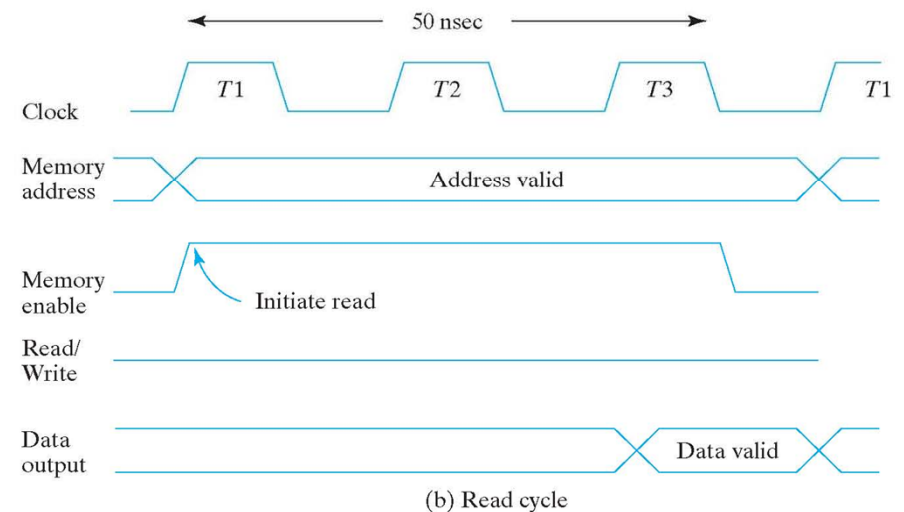- Read operation does not need CP to read data



Source: Digital Design, Frank Vahid, 1st ed, 2006



<http://www.cs.ucr.edu/~vahid/dd>

Memory: Reading and Writing

Write operation needs CP to write data

Read operation does not need CP to read data

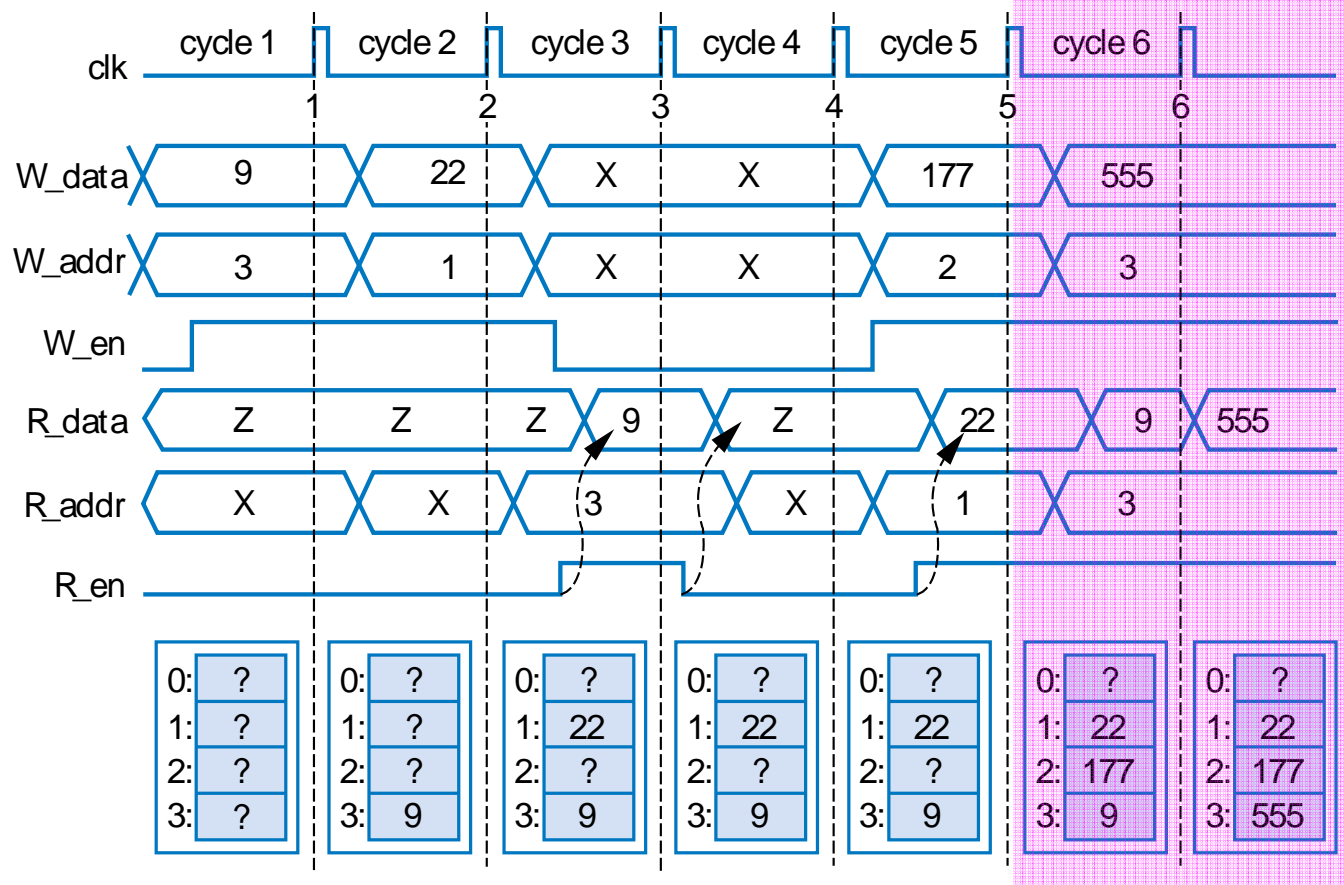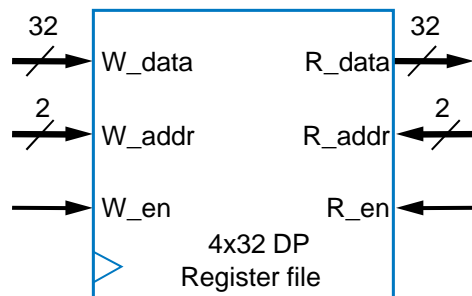****Dual-port RAM => can read and write simultaneously**





Reading may be done in the middle of a CP (instant)

Source: Digital Design, Mano and Ciletti, 4E, ISBN: 0131989243


Address Multiplexing

  - What about 1K x 1 (1024x1) memory?
- To decode the addresses, we require 10 bits
 - One 10x1024 decoder?
 - $1024 = 32 \times 32$
 - Rearrange 1024 memory cells as 32 x 32 2-D array
 - Need just Two 5x32 decoders?
- Address multiplexing
 - Two-dimensional decoding




Expanding Capacity – by Word Size

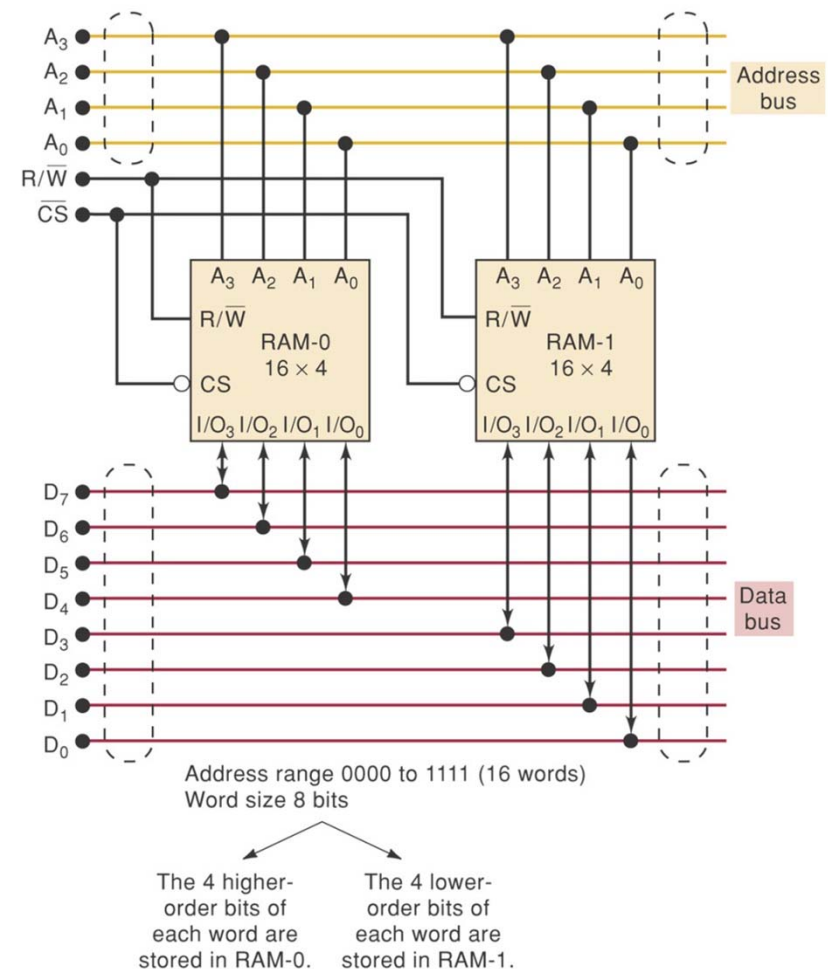- Expanding word size
- Combining RAMs
 - Two 16x4 RAM modules are combined for one 16x8 module (bit concatenation)
- What about one 32x4 module from 16x4 modules?




Expanding Capacity – by Address

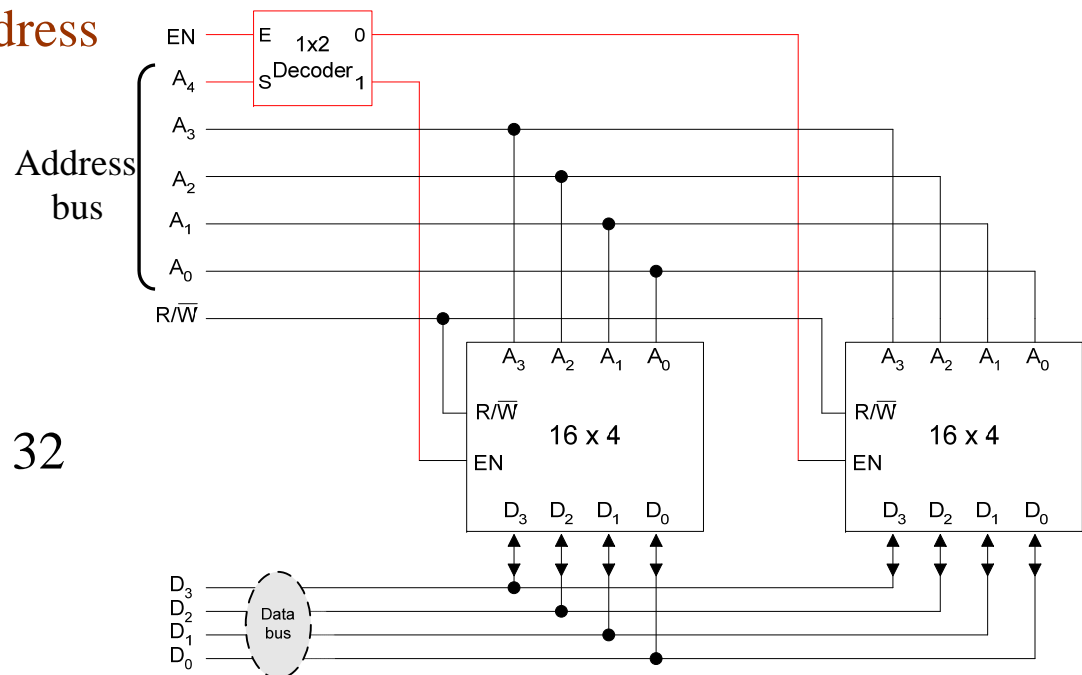- Expanding addresses (by **address multiplexing**)
- Combining RAMs
 - **Two 16x4 RAMs** are combined for **one 32x4 module**
 - **5 address lines** $\Rightarrow 2^5 \Rightarrow 32$ addresses
 - Here $EN = CS$
- Now design one **64x16** module using **16x4** RAM modules




****Note** that one **32x4 module** has the same capacity as one **16x8 module** (as size of both: 128 kbits = 16 bytes). However, they have entirely **different functionality** and are used for **different purposes**


64x16 Module using 16x4 Modules

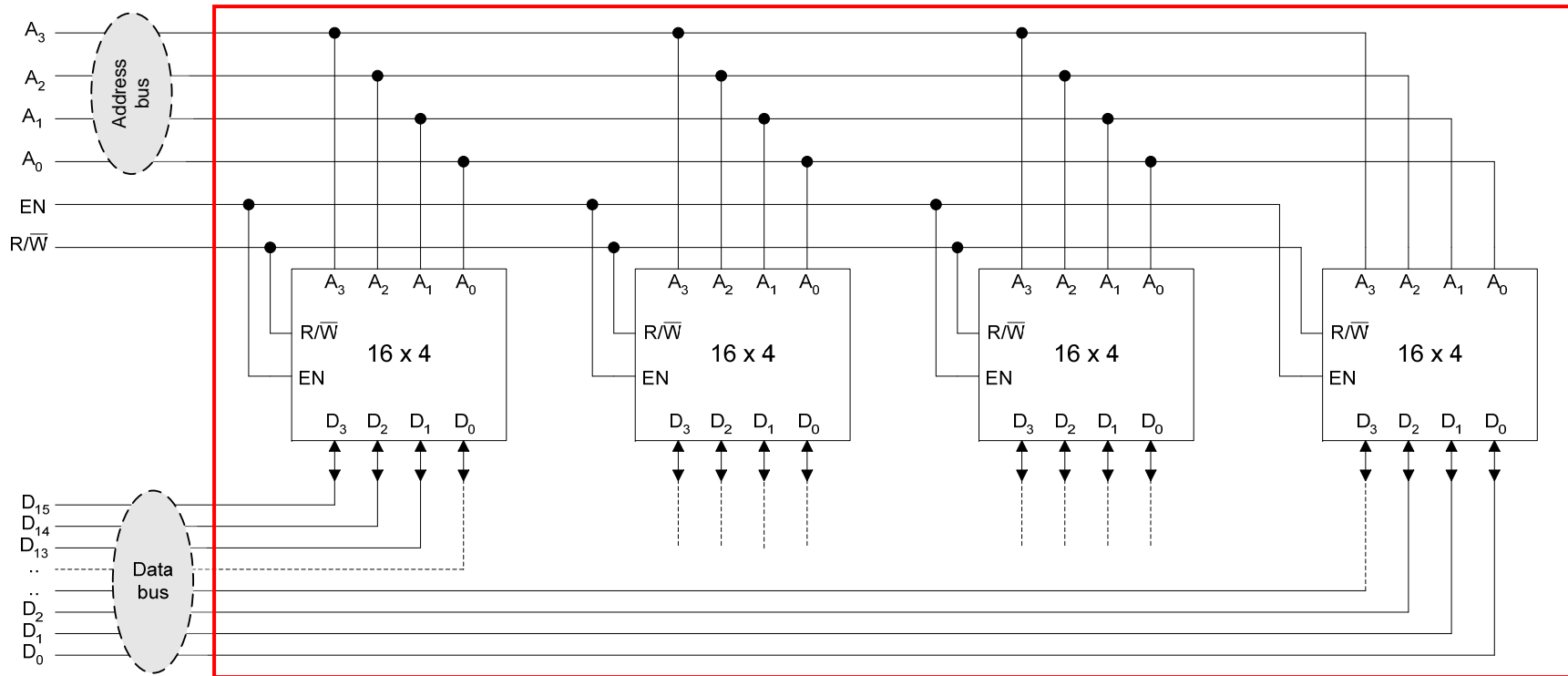

 First, design a 16x16 module by increasing the word size




64x16 Module using 16x4 Modules

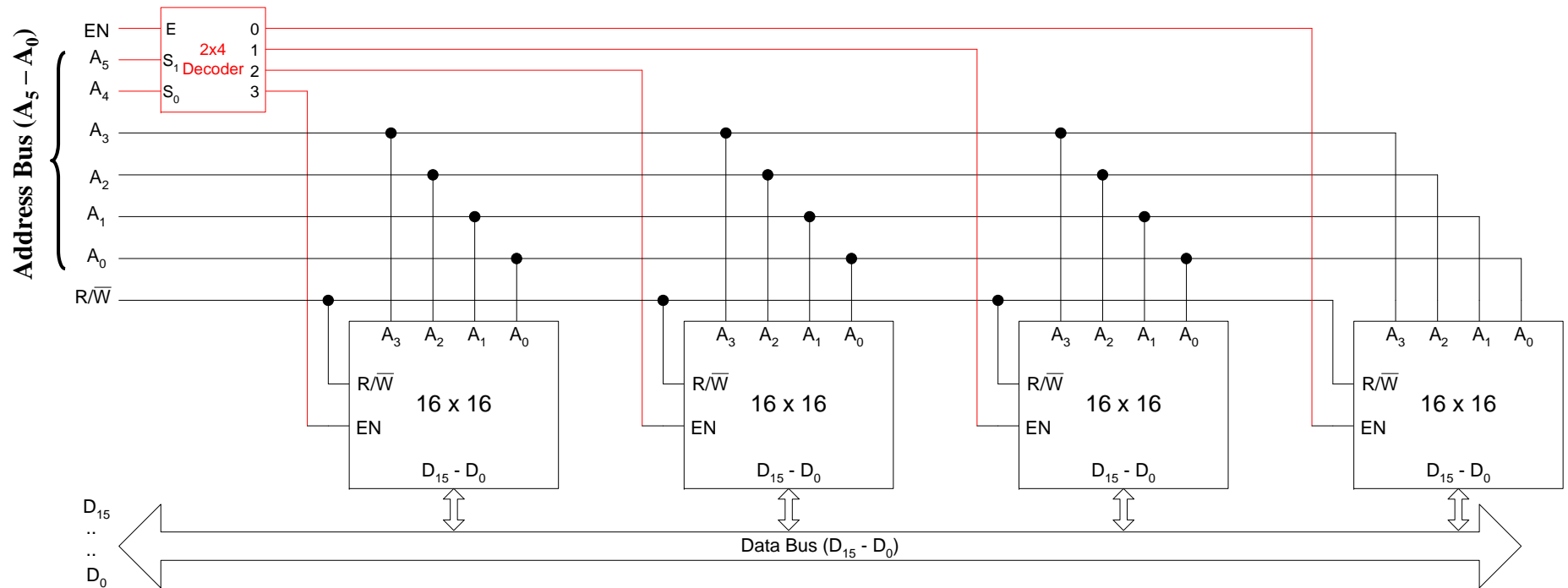

Now, **multiplex** the previously designed “16x16 module” to increase the address lines using **one 2x4 decoder**

 So we have **6 address lines** $\Rightarrow 2^6 \Rightarrow 64$ addresses




Source: Digital Systems: Principles and Applications, Tocci, Widmer and Moss, 10E, ISBN: 0131725793

S-RAM

□ Static Memory Devices:

 - Semiconductor memory in which the stored data will remain permanently stored as long as power is applied
- No refreshing (periodically rewriting the data into the memory)
- Requires more transistors
- BJT
 - High speed but very complex design
- MOS
 - Low power consumption, higher capacities



Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>

S-RAM – Operation

- S-RAM Operation - Writing
 - 6 transistors are required
 - *word enable* input comes from decoder
 - When $we = 0$, value d loops around inverters; that loop is where a bit stays stored
 - When $we = 1$, the *data* bit (“1” or “0”) value enters the loop
 - *data* is the bit to be stored in this cell
 - *data'* enters on other side
 - Example shows a “1” being written into cell

 


Figure 5.55 SRAM cell.

 


Figure 5.56 Writing a 1 to an SRAM cell.

Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>

S-RAM – Operation

- S-RAM Operation - Reading
 - Somewhat complicated and tricky
 - When *r/w* set to read, the RAM logic sets both *data* and *data'* to **1**
 - The stored bit *d* will pull either the left line or the right line down slightly below 1 depending on what is stored (here, right line is pulled down)
 - “Sense amplifiers” detect which side is slightly pulled down
 - The electrical description of SRAM is somewhat complex


 


Figure 5.57 Reading an SRAM.

D-RAM

- Dynamic Memory Devices:
 - Semiconductor memory in which the stored data will not remain permanently stored, even with power applied
 - Needs refreshing (periodically rewritten into memory)
 - In modern chips, common refresh rate: 7.8 μ sec, 15.6 μ sec, 31.2 μ sec, 64 μ sec, 128 μ sec, or Auto
 - Low power consumption, higher capacities
 - Requires less transistors
 - Moderate speed
 - Needs refreshing
 - DRAM is slower than SRAM

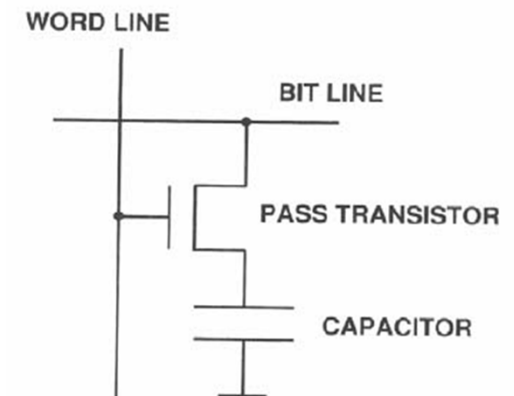

Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>

D-RAM – Operation

- D-RAM – Writing / Reading
 - 1 transistor (rather than 6 in SRAM)
 - Relies on *large* capacitor to store bit
 - **Write:** Transistor conducts, data voltage level gets stored on top plate of capacitor
 - **Read:** Just read the value of d
 - Problem:
 - Capacitor discharges over time
 - Must “refresh” regularly, by reading d and then writing it right back

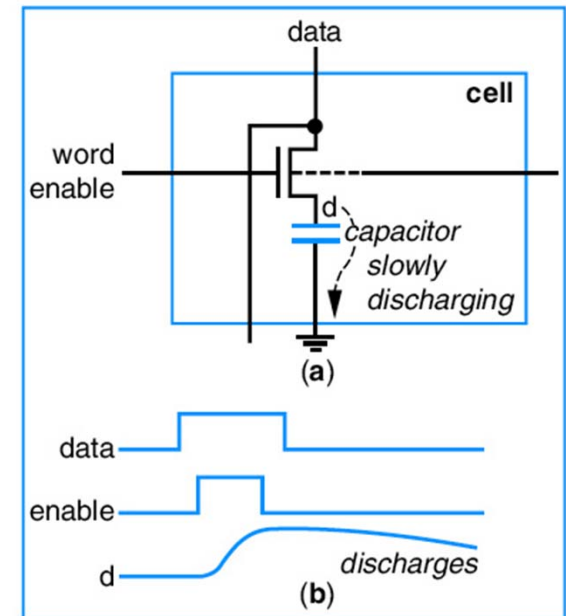


Figure 5.58 DRAM bit storage (a) bit storage block, (b) discharge.

More info: http://en.wikipedia.org/wiki/Dynamic_random_access_memory

D-RAM Types

- ❑ Memory modules
- ❑ FPM (Fast Page Mode) DRAM
- ❑ EDO (Extended Data Output) DRAM
- ❑ SDRAM (Synchronous DRAM)
- ❑ DDRSDRAM (Double Data Rate SDRAM)
- ❑ SLDRAM (Synchronous Link DRAM)
- ❑ DRDRAM (Direct Rambus DRAM)

Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>

RAM Comparisons

- Register file
 - Fastest
 - But biggest size
- SRAM
 - Fast
 - More compact than register file
- DRAM
 - Slowest
 - And refreshing takes time
 - But very compact, widely used
- Use register file for small items, SRAM for large items, and DRAM for huge items
 - Note: DRAM's big capacitor requires a special chip design process, so DRAM is often a separate chip

 



Figure 5.59 Depiction of compactness benefits of SRAM and DRAM (not to scale).

Source: Digital Design, Mano and Ciletti, 4E, ISBN: 0131989243

ROM Architecture

□ Three basic parts

 - **Register array** – stores data programmed into the ROM
- **Address decoders** – determines which register will be enabled by row and column
- **Output buffers** - pass data to the external data outputs
- Internal logical structure similar to RAM, without the data input lines
 - **No Input buffers**



This ROM is not programmed yet

Source: Digital Design, Mano and Ciletti, 4E, ISBN: 0131989243

Programming a ROM


ROM Truth Table (Partial)

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮						⋮				
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

Storing bits in a ROM
known as **programming**

Several programming methods

 - Mask-programmed ROM (MROM)
- One-Time Programmable ROM (OTPROM)
- Erasable PROM (EPROM)
- Electrically EPROM (EEPROM)



ROM Types

□ Mask-programmed ROM

- Bits are **hardwired** as 0s or 1s during chip manufacturing
- **Once programmed, can never be altered**
 - 2-bit word on the right stores “10”
- Word enable (from decoder) simply passes the hardwired value through transistor
- **The most compact** of any ROM type
- Best suited for high-volume well-established products

Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>


 


Figure 5.66 Mask-programmed ROM cells: left cell programmed with 1, right cell with 0.

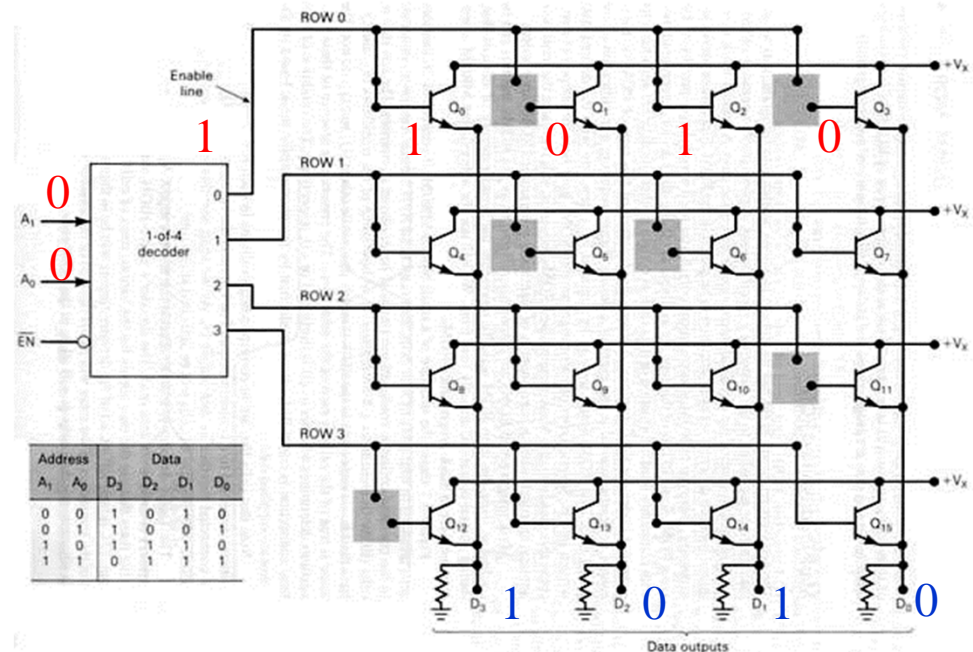

Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>

ROM Types

□ Fuse-Based Programmable ROM

- Each cell has a fuse
- A special device, known as a programmer, **blows certain fuses** (using higher-than-normal voltage)
 - **Blown cells will be read as 0s** (involves some special electronics)
 - **Unblown cells will be read as 1s**
 - 2-bit word on the right stores “10”
- Also known as **One-Time Programmable (OTP) ROM**
 - **Once programmed, can never be altered**

 


Figure 5.67 Fuse-based ROM cells: left cell programmed with 1, right cell with 0.

Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>

ROM Types

□ Erasable Programmable ROM (EPROM)

- Uses “*floating-gate transistor*” in each cell
- Special programmer device uses higher-than-normal voltage to cause electrons to tunnel into the gate
 - Electrons become trapped in the gate
 - Trapped cell stores 0
 - Non-trapped cell stores 1
 - 2-bit word on the right stores “10”
- To erase, shine **ultraviolet light** onto chip
 - Gives trapped electrons energy to escape
 - Requires chip package to **have a window**

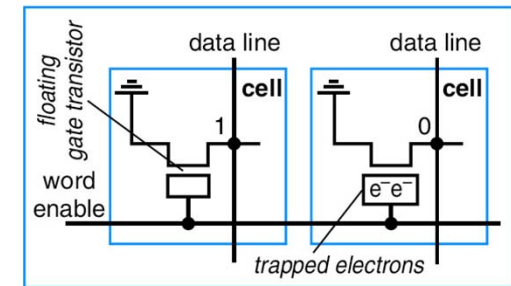


Figure 5.68 EPROM cells: left cell programmed with 1, right cell with 0.

 


Figure 5.69 The “window” in the package of a microprocessor that uses an EPROM to store programs.

Source: Digital Design, Frank Vahid, 1st ed, 2006

<http://www.cs.ucr.edu/~vahid/dd>

ROM Types

□ Electronically-Erasable Programmable ROM (EEPROM)

- Similar to EPROM – uses floating-gate transistor, electronic programming to trap electrons in certain cells
- But erasing is done electronically (no UV)
 - Erasing done one word at a time

□ Flash memory

- Similar to EEPROM, but all words (or large blocks of words) can be erased simultaneously
- Became very popular (after late 1990)
- Both types are in-system programmable
 - Requires bi-directional data lines, and write control input
 - Also need busy output to indicate that erasing is in progress – erasing takes some time

 


Figure 5.70 1024x32 EEPROM block symbol.

Source: Digital Design, Mano and Ciletti, 4E, ISBN: 0131989243


ROM Comparisons

In-circuit, electrically erasable
byte-by-byte

In-circuit, electrically erasable
by sector or in bulk (all cells)

UV erasable in bulk; erased and
reprogrammed out of circuit

Cannot be erased and
reprogrammed

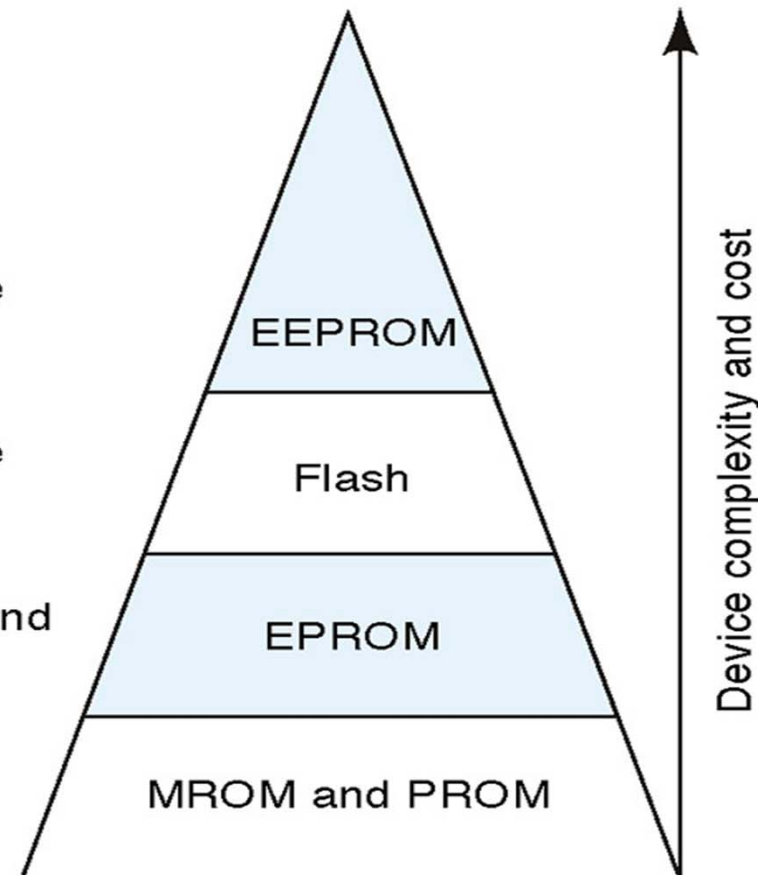

ROM Applications

□ Firmware

- Is in the storage of data and program codes that must be available immediately on power-up of computer/MCU systems
- MCU systems require this so that MPU can execute appropriate instructions to initiate the system and invoke an OS from auxiliary memory (bootstrap or booting) - BIOS
- EEPROM is often used to allow the firmware to be upgraded if necessary

□ Stored Data Tables

- To store tables of constant look-up data, e.g. trigonometric tables or code-conversion tables, etc.


ROM Applications

□ Auxiliary Storage

- Low cost flash memory is starting to become increasingly popular as an alternative form of auxiliary storage due to its high speed, low power requirements and lack of moving parts e.g. SDCARD, Compact flash cards, flash drive, etc.

□ Function Generator

 - By connecting the outputs of a ROM to a DAC and the address lines to a counter, pre-set voltage functions can be generated (a low pass filter is usually employed to smooth the analog output), e.g. speech synthesizer, etc.



Acknowledgments

- These slides have been prepared by Khan Wahid and may contain material copyrighted by:
 - **Digital Systems: Principles and Applications, Tocci, Widmer and Moss, 10E, ISBN: 0131725793**
 - **Digital Design, Frank Vahid, 1st ed, 2006**
 - **Fundamentals of Digital Logic with Verilog Design, Brown and Vranesic, 2E, ISBN: 9780073380339**
 - **Digital Design, Mano and Ciletti, 4E, ISBN: 0131989243**